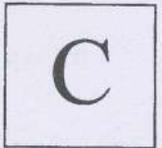


--	--	--	--	--	--	--	--



**B.Tech. Degree I Semester Regular/Supplementary Examination in
Marine Engineering November 2022**

**19-208-0105 BASIC ELECTRICAL ENGINEERING
(2019 Scheme)**

Time: 3 Hours


Maximum Marks: 60

Course Outcome

On successful completion of the course, the students will be able to:


- CO1: Acquire knowledge of electrical circuit analysis.
 - CO2: Review the basic concepts of magnetic circuits, electromagnetism & electrostatics.
 - CO3: Understand AC generation, representation & analysis of AC circuits.
 - CO4: Grasp the methods of Electrical power generation and concept of three phase system.
 - CO5: To understand Electrical power transmission, distribution, house wiring.
- Bloom's Taxonomy Levels (BL): L1 – Remember, L2 – Understand, L3 – Apply, L4 –Analyze, L5 – Evaluate, L6 – Create
PO – Programme Outcome

- | | | | | | |
|--------|---|-------|----|----|-------|
| | (5 × 15 = 75) | Marks | BL | CO | PO |
| I. (a) | Explain Kirchoff's voltage and current law. | 5 | L2 | 1 | 1.3.1 |
| (b) | Find mesh currents in the figure shown by mesh analysis. Apply Cramer's rule. | 10 | L5 | 1 | 2.2.2 |

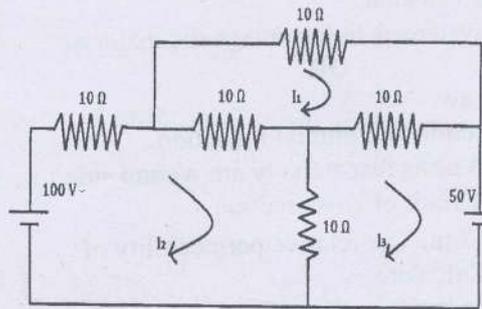


OR

- | | | | | | |
|---------|--|---|----|---|-------|
| II. (a) | Find the voltage across 2Ω resistor using superposition theorem. | 6 | L5 | 1 | 2.2.2 |
|---------|--|---|----|---|-------|

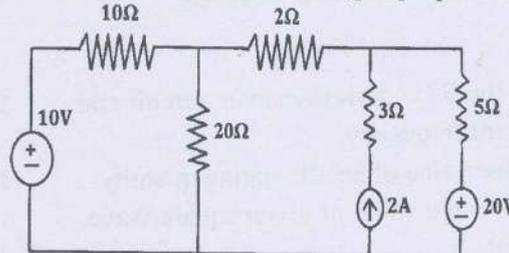


- | | | | | | |
|-----|--|---|----|---|-------|
| (b) | Using Thevenin's theorem, calculate the current flowing through 5 Ω resistor in the following circuit. | 4 | L5 | 1 | 2.2.2 |
|-----|--|---|----|---|-------|

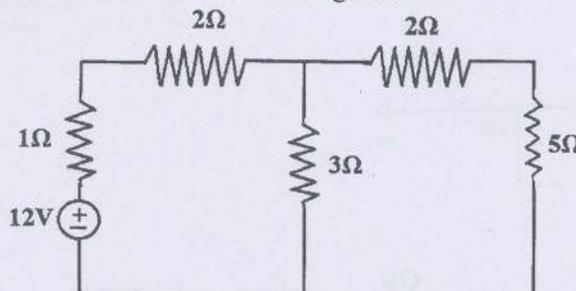


(c) Find the equivalent resistance between terminals 1 and 2, for the given circuit. Take $R_1 = R_2 = R_3 = 3\Omega$ and $R_{12} = R_{23} = R_{31} = 5\Omega$.

Marks	BL	CO	PO
5	L5	1	2.2.2

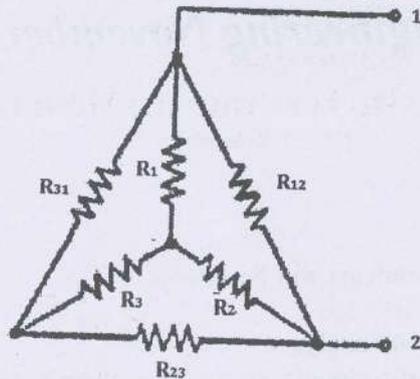

- | | | | | | |
|-----------|---|---|----|---|-------|
| III. (a) | State and explain Coulomb's law in electrostatics. | 3 | L1 | 2 | 1.3.1 |
| (b) | A steel ring of circular section 1cm in radius and having a mean circumference of 94.3 cm has an air gap of 1mm length. It is uniformly wound with 1000 turns of wire carrying a current of 2.5A. Calculate:
(i) MMF
(ii) Reluctance
(iii) Magnetic flux
(iv) Magnetic flux density in air gap
(v) Relative permeability of steel ring. Assume that steel path takes about 40% of the total mmf. | 8 | L3 | 2 | 2.2.2 |
| (c) | Explain the phenomenon of hysteresis in ferromagnetic material. | 4 | L2 | 2 | 1.3.1 |
| OR | | | | | |
| IV. (a) | State and explain Faraday's Law. | 4 | L1 | 2 | 1.3.1 |
| (b) | Distinguish between self induction and mutual induction. | 5 | L2 | 2 | 1.3.1 |
| (c) | Two coils having 150 and 200 turns respectively are wound side by side on a closed magnetic circuit of cross section $1.5 \times 10^{-2} m^2$ and mean length 3 m. The relative permeability of the magnetic circuit is 2000. Calculate:
(i) The mutual inductance between the coils
(ii) The voltage induced in the second coil if the current changes from 0 to 10A in the first coil in 20 ms. | 6 | L3 | 2 | 2.2.2 |
| V. (a) | What is resonance? Explain the RLC series resonant circuit and derive the equation for resonant frequency. | 5 | L2 | 3 | 1.3.1 |
| (b) | Define RMS value and average value of an alternating quantity. | 4 | L2 | 3 | 1.3.1 |
| (c) | Determine RMS value and average value of given square wave. Also find its peak and form factor. | 6 | L3 | 3 | 2.2.2 |

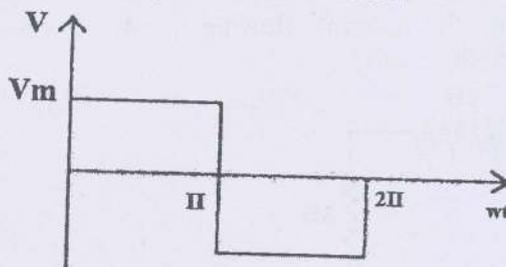

OR

(Continued)

BT MRE-I(R/S)-11-22-2017

	Marks	BL	CO	PO
VI. (a) Prove that average power for a purely capacitive circuit is zero.	5	L4	3	1.3.1
(b) A series circuit having $R = 100 \Omega$, $L = 0.12\text{H}$ and $C = 28.27\mu\text{F}$ is fed from 100 V, 50Hz supply. Find the current, active power, impedance, rms values of voltage across resistor, inductor and capacitor.	10	L5	3	2.2.2
VII. (a) Three impedances, each having resistance 20Ω and inductive reactance of 15Ω are connected in star connection across a 400V, three phase supply. Calculate: (i) The line current (ii) The power factor (iii) Total power in the circuit	6	L5	4	2.2.2
(b) Derive the relationship between line current and phase current in a three phase delta connected system with the help of vector diagram.	9	L2	4	1.3.1
OR				
VIII. (a) What factors are taken into account while selecting the site for thermal power plant? Also discuss the merits and demerits of thermal electric power plant.	5	L2	4	1.3.1
(b) Draw a neat schematic diagram of a hydro-electric power plant and explain the functions of various components. Also list four advantages and disadvantages.	10	L2	4	1.3.1
IX. (a) With the help of a diagram, explain the power transmission and distribution scheme.	9	L2	5	1.3.1
(b) Compare AC and DC transmission.	6	L2	5	1.3.1
OR				
X. (a) What is the purpose of earthing? Explain plate earthing in detail.	7	L2	5	1.3.1
(b) List out the important safety precautions that must be observed when working with electrical appliances.	8	L2	5	1.3.1

Bloom's Taxonomy Levels

L1 = 4.6%, L2 = 51.3%, L3 = 13.3%, L4 = 3.3%, L5 = 27.3%
