

--	--	--	--	--	--	--	--


**B.Tech. Degree I Semester Examination in
Marine Engineering December 2019**

**19-208-0105 BASIC ELECTRICAL ENGINEERING
(2019 Scheme)**


Time: 3 Hours

Maximum Marks: 60

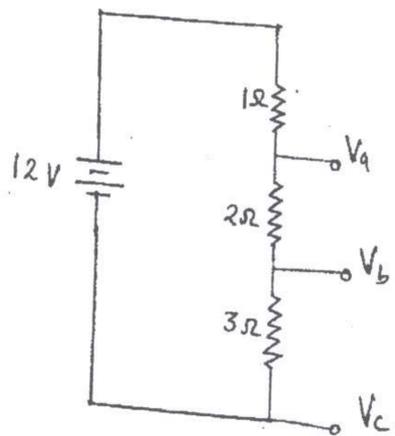- (5 × 15 = 75)
- I. (a) Find all the possible voltage values that can be obtained from the given circuit: (5)



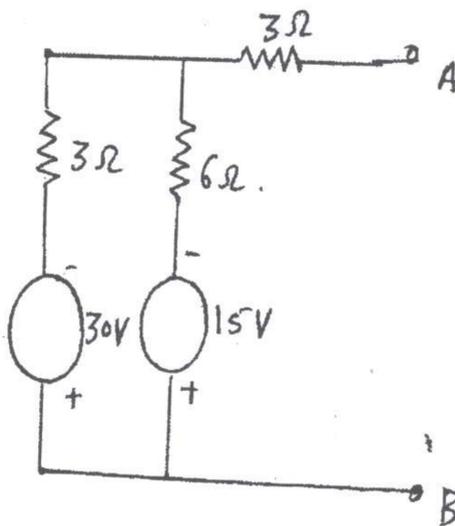
- (b) Find Thevenin's and Norton's equivalent of the following circuit: (5)



- (c) State Kirchoff's Laws (5)

OR

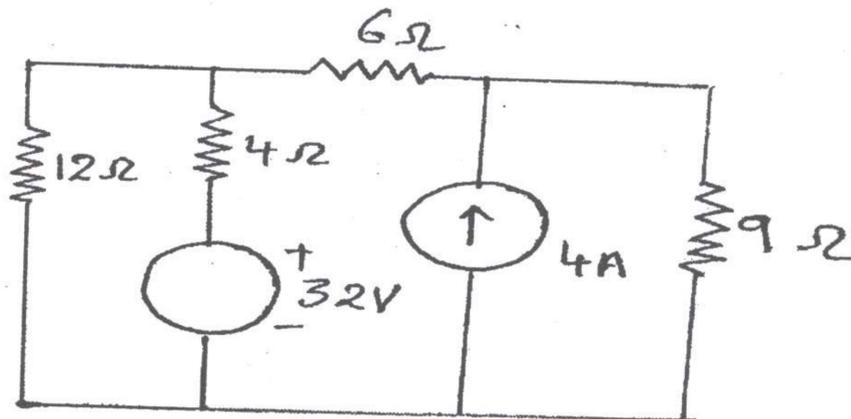- II. (a) Find Power in 9Ω by superposition theorem. (8)



- (b) State and illustrate Max power transfer theorem. (7)

- III. (a) Derive expression for energy stored in a capacitor. (7)
 (b) A ring composed of three sections. The cross-sectional area is 0.001m^2 for each section. The mean arc length are $l_a=0.3\text{m}$, $l_b = 0.2\text{m}$, $l_c = 0.1\text{m}$. An air-gap length of 0.1mm is cut in the ring. μ_r for sections a, b, c are 5000, 1000 and 10000 respectively. Flux in the air gap is 75mwb . (8)
 Find (i) mmf, (ii) exciting current if coil has 100 turns, (iii) reluctances of the sections.
- OR**
- IV. (a) State Faraday's law of Electromagnetic induction and Lenz's law (7)
 (b) Two coils have a mutual inductance of 0.3H . If the current in one coil is varied from 5A to 2A in 0.4s , calculate the average emf induced in the second coil, the change of flux linked with the second coil assuming that it is wound with 200 turns. (8)
- V. (a) Explain resonance in series RLC circuit. (7)
 (b) An R-L series circuit draws a current of 1A when connected across a 10V , 50Hz ac supply. Assuming the resistance to be 5Ω , find the inductance of the circuit. What is its power factor? (8)
- OR**
- VI. (a) Define the following terms with respect to an AC quantity: (7)
 (i) RMS value
 (ii) Frequency
 (iii) Form factor
 (iv) Average value
 (b) A series RLC circuit consists of $R = 1000\Omega$, $L = 100\text{mH}$ and $C = 10\text{picofarads}$. Applied voltage to the circuit is 100V . (8)
 Find: (i) Resonant frequency of circuit (ii) Quality factor of circuit at resonant frequency (iii) at what angular frequencies do half power points occur (iv) Bandwidth of circuit.
- VII. (a) Compare Thermal and Hydro power stations. (7)
 (b) A delta connected balanced 3 phase load when supplied from a 400V 50Hz 3 phase supply, draw a line current of 20A and the power taken by load is 10000W . Find (i) impedance in each branch (ii) line current and power if same load connected in star. (8)
- OR**
- VIII. (a) Derive the expression for three phase delta connected balanced load. (7)
 (b) Three phase star-connected load when supplied from a 400V , 50Hz source takes a line current of 10A at 66.86 degree with respect to its line voltage. (8)
 Calculate: (i) Impedance, (ii) pf and active power consumed.
 Draw phasor diagram.
- IX. (a) State the advantages of AC over DC transmission. (7)
 (b) Explain Plate Earthing with neat labelled diagram. (8)
- OR**
- X. (a) Explain briefly Ring main, radial and interconnected distribution system. (7)
 (b) Write notes on: (i) Fuse and its types (ii) MCB (5)
 (c) What are the points to be earthed in electrical distribution system. (3)