

B. Tech Degree I & II Semester Examination in Marine Engineering, May 2008

MRE 107 FUNDAMENTALS OF ENGINEERING I


(B) ELECTRICAL ENGINEERING

Time : 1 ½ Hours

Maximum Marks : 50


- I. (a) State and explain :
- (i) Kirchoff's current law
 - (ii) Kirchoff's voltage law
 - (iii) Ohm's law
 - (iv) Norton's theorem.
- (10)

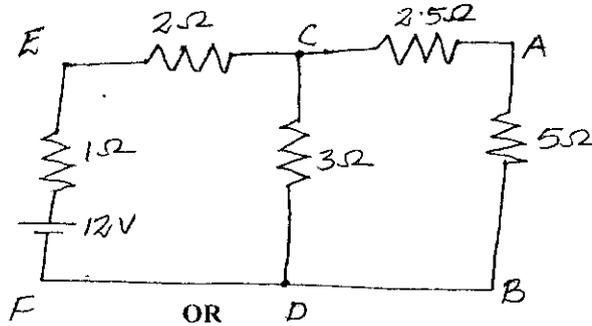- (b) Using Thevenin's theorem, calculate the current flowing through 5Ω resistor in the following circuit. (8)



- II. (a) State and explain :
- (i) Maximum power transfer theorem
 - (ii) Super position principle.
- (10)

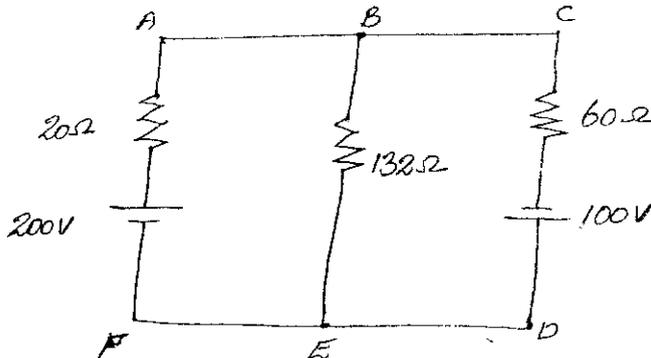- (b) For the network shown in the following figure, calculate the current in the 132Ω resistor and the potential difference across the 20Ω resistor by using Kirchoff's laws. (8)



- III. (a) State and explain the Coulomb's law in electrostatics. (3)
- (b) Define :
- (i) Capacitance
 - (ii) Electric flux density
 - (iii) Electric field strength.
- (3)

(Turn Over)

- (c) A capacitor consists of two metal plates each 40 cm x 40 cm spaced 6 mm apart. The space between the metal plates is filled with a glass plate 5 mm thick and a layer of paper 1 mm thick. The relative permittivities of glass and paper are 8 and 2 respectively. Calculate –
- the capacitance
 - the potential gradient in each dielectric in KV/mm due to a potential difference of 10 KV between the metal plates. Neglect any fringing flux.

(10)

OR

- IV. (a) Define self induction and mutual induction. (4)
- (b) State and explain Faraday's laws of electromagnetic induction. (4)
- (c) A ring-shaped electromagnet, which is uniformly wound with a magnetizing coil of 500 turns, has an air gap 6 mm long and 20 cm^2 in area, the mean length of the core being 50 cm. A current of 5 A in the coil produces a flux density of 0.5 Wb/m^2 in the air gap. Find the relative permeability of iron at this flux density. (8)

- V. (a) Define the following with respect to alternating current/voltage :
- Frequency
 - Phase difference
 - RMS value
 - Average value
 - Power factor
 - Form factor
- (b) Find vectorically the resultant of the following four voltages : (9)

$$e_1 = 25 \sin \omega t \quad e_2 = 30 \sin \left(\omega t + \frac{\pi}{6} \right)$$

$$e_3 = 30 \cos \omega t \quad e_4 = 20 \sin \left(\omega t - \frac{\pi}{4} \right)$$

Express the answer in a similar form. (7)

OR

- VI. (a) What is resonance? Explain the RLC series resonant circuit and derive the equation for resonant frequency. (6)
- (b) An inductor of 0.5 H inductance and 90Ω resistance is connected in parallel with a $20 \mu\text{F}$ capacitor. A voltage of 230 V 50 Hz is maintained across the circuit. Determine the total power taken from the source. (5)
- (c) Three Δ - connected similar coils when supplied from a 416 V 50 Hz 3 phase 3 wire supply, draw a line current of 5 A at a p.f. of 0.8 lag. Calculate the resistance and inductance of each coil. (5)

