

B. Tech Degree I & II Semester Examination in Marine Engineering June 2011

MRE 107 FUNDAMENTALS OF ENGINEERING – I

PART- B ELECTRICAL ENGINEERING


Time : 1 ½ Hours

Maximum Marks : 50

- I. a) Derive the expression to obtain the effective resistance of n resistors connected in parallel. (4)
- b) A direct current circuit comprises two resistors, A of 25 ohms, and B of unknown value connected in parallel, together with a third resistor C of value 5 ohms connected in series with the parallel group. The potential difference across c is found to be 90V. If the total power in the circuit is 4320 W, calculate: (10)
- i) the value of resistor B
 - ii) the voltage applied to the ends of the whole circuit,
 - iii) the current in each resistor
- c) What are ideal voltage and current sources? (4)

OR

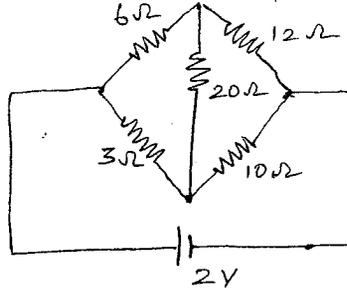- II. a) State and explain Thevenin's theorem. (6)
- b) Determine the current in 20Ω resistor of the network shown in figure by Thevenin's theorem. (12)



- III. a) State coulomb's law of electro statics. (4)
- b) Derive the expression for capacitance of a parallel plate capacitor. (4)
- c) An iron ring has a cross section of 3cm^2 and a mean diameter of 25cm. An air gap of 0.4mm has been cut across the section of the ring. The ring is around with a coil of 200 turns through which a current of 2A is passed. If the total magnetic flux is 0.24 mwb, find the relative permeability of iron assuming no magnetic leakage. (8)

OR

- IV. a) Explain the following: (6)
- i) Hysteresis
 - ii) Fringing
- b) Distinguish between self inductance and mutual inductance. (4)
- c) Two coils having 150 and 200 turns respectively are wound side by side on a closed magnetic circuit of cross section $1.5 \times 10^{-2} \text{ m}^2$ and mean length 3m. The relative permeability of the magnetic circuit is 2000. Calculate: (a) the mutual inductance between the coils; (b) the voltage induced in the second coil if the current changes from 0 to 10A in the first coil in 20ms. (6)

- V. a) Explain the generation of alternating voltages. (8)
- b) Define the following terms: (8)
- i) time period
 - ii) Power factor
 - iii) Form factor
 - iv) r.m.s value

OR

- VI. a) Prove that the active power over a complete cycle in a purely inductive circuit is zero. (6)
- b) A coil of resistance 10Ω and inductance of 0.02H is connected in series with another coil of resistance 6Ω and inductance of 15mH across a 230V , 50Hz supply. Calculate (i) the impedance of the circuit (ii) the voltage drop across each coil and (iii) the total power consumed by the circuit. (10)