


# B.Tech Degree I&II Semester Examination in Marine Engineering June 2012

## MRE 107 FUNDAMENTALS OF ENGINEERING I (B) ELECTRICAL ENGINEERING

Time : 1½ Hours

Maximum Marks : 50

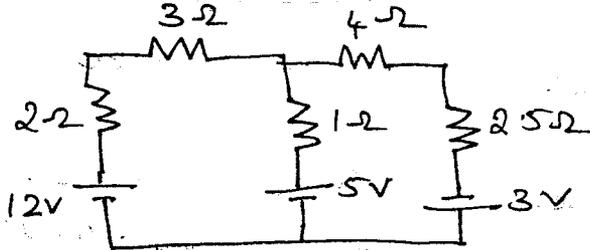- I. (a) State and explain kirchoff's laws for an electric circuit. (6)  
 (b) (10)




Using Kirchoff's laws determine

- (i) current in the 2.5 Ω resistor  
 (ii) voltage across 1 Ω resistor, for the circuit shown in figure.

OR

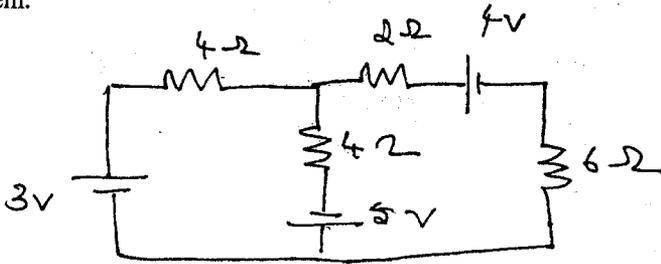- II. (a) State and explain maximum power transfer theorem. (6)  
 (b) For the circuit shown in figure, calculate the current in the 6 Ω resistor using Norton's theorem. (10)



- III. (a) State and explain Coloumb's law. (6)  
 (b) A magnetic core in the form of a closed ring has a mean length of 20cm and a cross section of 1cm<sup>2</sup>. The relative permeability of iron is 2400. What direct current will be needed in a coil of 2000 turns uniformly wound the ring to create a flux of 0.2 mwb in the iron. (12)

OR

- IV. (a) State and explain Faraday's law. (8)  
 (b) Two coils have a mutual inductance of 0.3H. If the current in one coil is varied from 5A to 2A in 0.4s, calculate: (10)  
 (i) the average run of induced in the second coil.  
 (ii) The change of flux linked with the second coil assuming that it is wound with 200 turns

- V. (a) Define rms value and average value of an alternating current. Obtain the rms value of a sinusoidal quantity. (8)  
 (b) A series circuit consists of a 300 Ω non inductive resistor, a 7.95 μ F capacitor and a 206 H inductor of negligible resistance. If the supply voltage is 250V at 50 Hz, calculate: (8)  
 (i) impedance (ii) circuit current (iii) phase angle (iv) voltage, across each element.

OR

- VI. (a) Define the terms: (8)  
 (i) cycle (ii) frequency (iii) amplitude (iv) time period  
 (b) With the aid of a phasor diagram obtain the relationship between the line and phase values of voltage in a three phase star connected system. (8)