

--	--	--	--	--	--	--	--	--	--

***B. Tech. Degree III Semester Examination in  
Marine Engineering December 2016***

**MRE 1302 ELECTRICAL TECHNOLOGY  
(2013 Scheme)**

Time: 3 Hours

Maximum Marks: 100

(5 × 20 = 100)

- I. (a) Draw and explain the phasor diagram of a single phase transformer under lagging load. (6)
- (b) A 3300/300V single phase transformer gives 0.6 A and 60 W as ammeter and watt meter readings when supply is given to the low voltage windings and high voltage winding is kept open. Find: (7)
- (i) Power factor of no load current.
- (ii) Magnetising component (iii) Iron loss component.
- (c) Develop the exact equivalent circuit of a single phase transformer. From this derive the approximate and simplified equivalent circuit of the transformer. State the various assumptions made. (7)

OR

- II. (a) State and prove the condition for maximum efficiency. (5)
- (b) Derive an expression for saving in conductor material in an auto transformer over a two winding transformer of equal rating. (5)
- (c) A transformer is rated at 100 KVA. At full load its copper loss is 1200 W and its iron loss is 960 W. Calculate: (10)
- (i) the efficiency at full load unity power factor.
- (ii) the efficiency at half full load, 0.8 power factor.
- (iii) the efficiency at 75% full load 0.7 power factor.
- (iv) the load KVA at which maximum efficiency occur.
- (v) the maximum efficiency at 0.85 power factor.

- III. (a) A shunt generator supplied 500 A at 500 V. Calculate its generated emf if its armature and shunt field resistances are  $0.02\Omega$  and  $125\Omega$  respectively. (5)
- (b) What are the conditions for building up of voltage in a dc shunt generator? (5)
- (c) What are the effects of armature reaction in a dc generator? (3)
- (d) A short shunt compound generator has armature, series field and shunt field resistances of  $0.06\Omega$ ,  $0.03\Omega$  and  $110\Omega$  respectively. It supplies 100 lamps rated at 250 V, 40 W. Find the generated emf. Assume that contact drop/brush = 1 V. (7)

OR

- IV. (a) Derive the torque equation of a dc motor. (5)
- (b) DC series motor never started on no load. Explain why. (5)
- (c) A 500 V dc shunt motor takes 8 A on no load. The armature and field resistances are  $0.2\Omega$  and  $250\Omega$  respectively. Find the efficiency of the machine: (10)
- (a) When run as a motor taking a line current of 90 A at 500 V.
- (b) When run as a generator delivering a current of 90 A at 500 V.

- V. (a) Sketch the torque-slip characteristic of a 3 phase induction motor indicating the starting torque, maximum torque and operating region. How do the starting and maximum torque vary with rotor resistance? (8)
- (b) A 3 phase 6-pole, 50 Hz induction motor has 160 N-m as its useful full load torque. The rotor emf is observed to make 90 cycles per minute. Calculate: (12)
- (i) Motor output in KW (ii) Copper losses in rotor (iii) Motor input  
(iv) Efficiency if mechanical torque lost in friction and windage is 20 N-m and stator losses are 80 W.

**OR**

- VI. (a) Describe with diagram the working of a star-delta starter. (7)
- (b) A 3 phase 4 pole, 50 Hz induction motor is running at 1440 rpm. Determine the slip speed and slip. (3)
- (c) Describe with the help of connection diagrams and phasor diagrams of two methods of producing starting torque in a single phase induction motor. (10)
- VII. (a) A 3 phase 16 pole synchronous generator has a resultant flux of 0.06 Wb per pole. The flux is distributed sinusoidally over the pole. The stator has 2 slots per pole per phase and 4 conductors per slot. The coil span is  $150^\circ$ . Calculate the phase and line voltages when the machine runs at 375 rpm. (10)
- (b) A 600 V, 60 KVA single phase alternator has an effective resistance of  $0.2\Omega$ . A field current of 10 A produces an armature current of 210 A on short circuit and an emf of 480 V on open circuit. Calculate: (10)
- (i) Synchronous impedance and reactance.  
(ii) Full load regulation with 0.8 pf lagging.

**OR**

- VIII. (a) Draw the phasor diagrams of an alternator at unity, lagging and leading power factors. (6)
- (b) Explain what is a synchronous condenser with phasor diagram. (6)
- (c) A 200 V, 3 phase star connected synchronous motor has a resistance per phase of  $0.2\Omega$  and a synchronous reactance per phase of  $2.2\Omega$ . Determine the value of generated emf when the input is 800 KW at 0.8 power factor lagging. (8)
- IX. (a) Explain 3 wire dc system of distribution of electrical power. (6)
- (b) Draw a single line diagram showing a typical distribution system. (6)
- (c) Explain the following systems of distribution. (8)
- (i) Ring main system (ii) Inter connected system.

**OR**

- X. (a) Discuss the principle of operation of an air blast circuit breaker. What are the advantages and disadvantages of using air as the arc quenching medium? (10)
- (b) Write short notes on the following. (10)
- (i) Semi-enclosed rewirable fuse.  
(ii) HRC cartridge fuse.