

| | | | | | | | |
|--|--|--|--|--|--|--|--|
| | | | | | | | |
|--|--|--|--|--|--|--|--|

B.Tech. Degree III Semester Regular/Supplementary Examination in Marine Engineering November 2022

**19-208-0304 MARINE ELECTRONICS
(2019 Scheme)**

Time: 3 Hours

Maximum Marks: 60

Course Outcome

On successful completion of the course, the students will be able to:

- CO1: Understand the circuit and working of Power amplifiers, Operational Amplifiers and linear Op-amp circuits.
- CO2: List and explain the different number system and their conversions, binary codes and Boolean algebra. To acquire knowledge on logic gates and its application in digital circuits like multiplexers, flip-flops, counters and registers.
- CO3: Learn analog to digital converters and digital to analog converters and basic programming of 8085 microprocessor
- CO4: Understand the basic structure and working of semiconductor memories and Industrial electronics devices.
- CO5: Gain basic knowledge on communication system and its application in different communication system.
- Bloom's Taxonomy Levels (BL): L1 – Remember, L2 – Understand, L3 – Apply, L4 – Analyze, L5 – Evaluate, L6 – Create
- PO – Programme Outcome

| | | (5 × 15 = 75) | Marks | BL | CO | PO |
|-----------|--|---------------|-------|----|----|-------|
| I. | (a) With a neat circuit explain Class B power Amplifier. | 7 | | L1 | 1 | 1.3.1 |
| | (b) Elaborate on ideal Op-Amp Characteristics. | 8 | | L1 | 1 | 1.3.1 |
| OR | | | | | | |
| II. | (a) What is the effect of feedback in Op-Amps? Draw and explain inverting type of op-amp and find its gain equation. | 7 | | L1 | 1 | 1.3.1 |
| | (b) Explain CMRR and slew rate with neat circuits. | 8 | | L2 | 1 | 1.3.1 |
| III. | (a) Reduce the following expressions using Boolean postulates, laws and axioms. $(A + B + C)(A + B + \overline{C}) + (A + B)(A + C)$. | 6 | | L3 | 2 | 1.3.1 |
| | (b) What is flip flop? Explain S-R flip flop. Which flip flop is used to make counters and why? Explain 3-bit negative edge triggered Up counter using suitable flip flop. | 9 | | L3 | 2 | 1.3.1 |
| OR | | | | | | |
| IV. | (a) Explain Multiplexers. Write the expressions and truth table for 4:1 MUX and implement it using gates. Implement the logic function using MUX $F = \sum m(1,2,3,4,7)$ and draw its truth table. | 9 | | L4 | 2 | 1.3.1 |
| | (b) Perform 1's and 2's complement subtraction $(14.75)_{10} - (15.5)_{10}$. | 6 | | L3 | 2 | 1.3.1 |
| V. | (a) Draw and explain the architecture of 8085 microprocessor. | 8 | | L1 | 3 | 1.3.1 |
| | (b) Write an assembly language program to find the square root (take account only perfect squares) of a number stored at memory location 8080H and store the result at 8081H. | 7 | | L3 | 3 | 1.3.1 |
| OR | | | | | | |
| VI. | (a) Explain successive approximation type ADC. | 7 | | L1 | 3 | 1.3.1 |
| | (b) Elaborate on 3-bit R-2R ladder type DAC. | 8 | | L2 | 3 | 1.3.1 |

(P.T.O.)

BT MRE-III(R/S)-11-22-2022

| | | Marks | BL | CO | PO |
|-------|---|-------|----|----|-------|
| VII. | Discuss how can you store and retrieve a word from RAM, ROM and PROM. | 15 | L1 | 4 | 1.3.1 |
| | OR | | | | |
| VIII. | (a) Explain CMOS NAND gate. | 7 | L1 | 4 | 1.3.1 |
| | (b) How SCR can act as a rectifier? | 8 | L1 | 4 | 1.3.1 |
| IX. | (a) What is modulation? Explain the need of modulation. Elaborate on types of modulation. | 8 | L1 | 5 | 1.3.1 |
| | (b) With a neat block diagram explain super heterodyne receiver. | 7 | L1 | 5 | 1.3.1 |
| | OR | | | | |
| X. | Explain satellite communication as applicable to GMDSS. | 15 | L1 | 5 | 1.3.1 |

Bloom's Taxonomy Levels
 L1 = 65%, L2 = 10%, L3 = 19%, L4 = 6%
