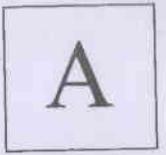


--	--	--	--	--	--	--	--	--	--



## ***B.Tech. Degree III Semester Regular/Supplementary Examination in Marine Engineering November 2023***

**19-208-0304 MARINE ELECTRONICS  
(2019 Scheme)**

Time: 3 Hours

Maximum Marks: 60

**Course Outcome**

On successful completion of the course, the students will be able to:

- CO1: Understand the circuit and working of Power amplifiers, Operational Amplifiers and linear Op-amp circuits.
- CO2: List and explain the different number system and their conversions, binary codes and Boolean algebra. To acquire knowledge on logic gates and its application in digital circuits like multiplexers, flip-flops, counters and registers.
- CO3: Learn analog to digital converters and digital to analog converters and basic programming of 8085 microprocessor
- CO4: Understand the basic structure and working of semiconductor memories and Industrial electronics devices.
- CO5: Gain basic knowledge on communication system and its application in different communication system.
- Bloom's Taxonomy Levels (BL): L1 – Remember, L2 – Understand, L3 – Apply, L4 –Analyze, L5 – Evaluate, L6 – Create
- PI – Programme Indicators

Answer **ALL** questions

(5 × 15 = 75)

		Marks	BL	CO	PI
I.	(a) Differentiate Class A and Class B power amplifiers.	7	L1	1	1.3.1
	(b) Explain the concept of Differential Amplifiers.	8	L1	1	1.3.1
<b>OR</b>					
II.	(a) Elaborate on input offset voltage, CMRR and slew rate of an Op-Amp.	7	L1	1	1.3.1
	(b) Explain any two linear Op-Amp Circuits with neat circuit diagrams.	8	L2	1	1.3.1
III.	(a) Convert $(37.93)_{10}$ to octal form.	3	L3	2	1.3.1
	(b) What is gray code? Convert $(5A)_{16}$ to gray code.	3	L3	2	1.3.1
	(c) Explain De-Morgan's theorem and Duality principle. Minimise the expression using Boolean postulates and laws.	9	L3	2	1.3.1
$F = \overline{ABC} + B + B\overline{D} + AB\overline{D} + \overline{AC}$					
<b>OR</b>					
IV.	(a) What are registers? Which flipflop is used to make registers and Why? Explain PISO shift registers.	10	L4	2	1.3.1
	(b) Explain JK flip-flop? Elaborate the condition when JK = 11.	5	L3	2	1.3.1

(P.T.O.)

BT MRE-III(R/S)-11-23-3009

		Marks	BL	CO	PI
V.	(a) Explain the terms Quantization and Sampling. Draw and explain any one analog to digital converter.	10	L1	3	1.3.1
	(b) Explain flag register of 8085 microprocessor with an example.	5	L2	3	1.3.1
<b>OR</b>					
VI.	(a) Write an assembly language program to find whether the given 8 bit number located at memory 9000H is even or odd. If even store ABH at 9001H else store BAH at 9001H.	7	L3	3	1.3.1
	(b) Elaborate on different registers, interrupts, data bus and control bus in 8085 microprocessor.	8	L1	3	1.3.1
VII.	Write a short note on Semiconductor memories.	15	L1	4	1.3.1
<b>OR</b>					
VIII.	(a) With a neat circuit explain CMOS NAND gate.	9	L2	4	1.3.1
	(b) How SCR performs rectification.	6	L2	4	1.3.1
IX.	(a) Explain the block diagram of monochrome TV transmitter and receiver.	10	L1	5	1.3.1
	(b) Explain Pulse modulation.	5	L1	5	1.3.1
<b>OR</b>					
X.	(a) With a neat block diagram explain AM transmitter and receiver.	10	L1	5	1.3.1
	(b) Comment the advantages of using high frequency carrier signal in modulation.	5	L2	5	1.3.1

Bloom's Taxonomy Levels

L1 = 53.33%, L2 = 22%, L3 = 18%, L4 = 6.67%.

\*\*\*