

--	--	--	--	--	--	--	--	--	--

***B.Tech. Degree IV Semester Examination in  
Marine Engineering May 2017***

**MRE 1404 MARINE ELECTRONICS  
(2013 Scheme)**

Time: 3 Hours

Maximum Marks: 100

(5 × 20 = 100)

- I. (a) What is a power amplifier? Explain the different performance parameters of power amplifiers. (10)  
 (b) With neat diagram, explain the working of push-pull amplifier. What are its advantages and disadvantages? (10)
- OR**
- II. (a) Draw and explain the circuit of a differential and a non-inverting amplifier. Derive the gain equations for these circuits. (10)  
 (b) Explain the following terms with respect to an Op-Amp. (10)  
 (i) CMRR  
 (ii) Slew rate  
 (iii) Input offset voltage  
 (iv) Input bias current  
 (v) Gain
- III. (a) Draw and explain SISO and PIPO shift registers. (10)  
 (b) Explain any one ADC using neat diagrams. (10)
- OR**
- IV. (a) What are universal gates? Implement the AND, OR, NOT and XOR gates using universal gates. (10)  
 (b) Reduce using K-map: (10)  

$$F = \sum m(1,2,6,7,8,13,14,15) + d(3,5,12)$$
- V. (a) Explain how a NAND gate is realized using TTL and CMOS circuits. (10)  
 (b) Write short notes on ROM, RAM, and PROM. (10)
- OR**
- VI. (a) Explain the V-I characteristics of SCR. (10)  
 (b) Explain with neat diagrams and waveforms a half wave rectifier using SCR. (10)
- VII. (a) Write short notes on pulse communication. (10)  
 (b) Write short note on satellite communication. (10)
- OR**
- VIII. (a) Write short notes on AM, FM and PM. (10)  
 (b) What is modulation and demodulation? Explain the need for modulation. (10)
- IX. (a) Explain the architecture of 8085 microprocessor. (12)  
 (b) Write an assembly language program to Add two 8-bit numbers stored at locations 9000H and 9001H and store the sum at 9002H and carry at 9003H. (8)
- OR**
- X. (a) Explain the flag register and other registers in 8085 microprocessor. (10)  
 (b) Write an assembly language program to multiply two 8-bit numbers stored at locations 9000H and 9001H and store the result at 9002H. (10)