

--	--	--	--	--	--	--	--

***B.Tech. Degree IV Semester Examination in  
Marine Engineering June 2015***

**MRE 1404 MARINE ELECTRONICS**

Time : 3 Hours

Maximum Marks : 100

- I. (a) What are power amplifiers? How are they classified? Compare their collector efficiencies. (10)  
 (b) Explain the circuit and operation of a push-pull amplifier, with neat diagrams. What is the use of phase-inverter circuit in it? (10)
- OR**
- II. (a) Define with respect to an op-amp: (i) input offset voltage (ii) input bias current (iii) CMRR (iv) output voltage swing (v) slew rate. Give typical values of each for op-amp IC 741. (10)  
 (b) Draw and explain the circuits of inverting and non-inverting amplifiers using op-amp with feedback and derive the gain equations. (10)
- III. (a) What are universal gates? Explain. Implement AND, OR, NOT and XOR gates using universal gates. (10)  
 (b) State and prove De-Morgan's theorems. (5)  
 (c) Explain J-K flip flops and how it can be converted to T-flip flops. (5)
- OR**
- IV. (a) Draw the circuit diagram of a 3-bit up/down counter and explain it. (10)  
 (b) Explain any one type of ADC with neat diagrams. (10)
- V. (a) Draw and explain TTL and CMOS inverter circuits. (10)  
 (b) Write notes on semiconductor memories. (10)
- OR**
- VI. (a) Draw the circuit diagram and wave-forms of a phase-controlled full-wave rectifier. Explain its working. (10)  
 (b) Write notes on photo electric devices. (10)
- VII. (a) What is modulation and demodulation? What is the need for modulation in communication systems? (10)  
 (b) Differentiate between AM, FM and PM. (10)
- OR**
- VIII. (a) Draw and explain the working of a RADAR, with the help of a neat diagram. (10)  
 (b) Write short notes on PWM, PPM and PCM. (10)
- IX. (a) With neat diagrams, explain the architecture of 8085 microprocessor. (12)  
 (b) What are the different register pairs in 8085 microprocessor? Explain. (8)
- OR**
- X. (a) Write a program to add two hexadecimal numbers and to display the answer in an output port. (10)  
 (b) Briefly explain the different categories of instructions in 8085 microprocessor with examples. (10)